



End Term (Odd) Semester Examination December 2024

Roll no 24g2001

Name of the Course and semester: BCA / 3rd Sem

Name of the Paper: Digital Logic Design

Paper Code: TBC 303

Time: 3 hour

Maximum Marks: 100

Note:

- (i) All the questions are compulsory.
- (ii) Answer any two sub questions from a, b and c in each main question.
- (iii) Total marks for each question is 20 (twenty).
- (iv) Each sub-question carries 10 marks.

Q1.

(2X10=20 Marks) (CO 1)

a. Perform various conversion:

- i. $(20A4.95)_{16} = ()_8$
- ii. $(1145.86)_8 = ()_{16}$
- iii. $(72.22)_8 = ()_{10}$
- iv. $(1449.44)_{10} = ()_2$

b. Realize the AND, OR, NOT and EX-OR Gate using NAND gate only.

c. Explain 1's and 2's complement method. Find out the subtraction of given numbers by 2's complement method, i. $(1010)_2 - (0111)_2$ and ii. $(0101)_2 - (1100)_2$

Q2.

(2X10=20 Marks) (CO 2)

a. Explain and prove De Morgan's theorem using example. Also define Associative and Distributive Laws with example.

b. Perform the minimization of given function using k-map,
 $f(A, B, C, D) = \sum m(1, 3, 7, 11, 15) + \sum d(0, 2, 5, 8, 14)$.

c. Show the logic circuit for this Boolean equation $Y = (A' + B) \cdot (A + B)$. Then, simplify as much as possible using algebra. Simplify the following Boolean expressions:
 $(A' + B + C') \cdot (A' + B + C) \cdot (C + D) \cdot (C + D + E)$

Q3.

(2X10=20 Marks) (CO 3)

a. Explain the working of full adder with truth table and logic circuit diagram.

b. Design the 4-bit Binary to Gray code converter with neat diagram.

c. Differentiate between Encoder and Decoder. Also design 2 to 4 line decoder.

Q4.

(2X10=20 Marks) (CO 4)

a. Explain race around condition. Draw the circuit of S-R and J-K flip flop using NAND Gate and find out the truth table with equation of each flip flop.

b. Design and explain the working of 4 bit PISO shift registers with suitable diagram.



End Term (Odd) Semester Examination December 2024

- c. Design a 3-bit Synchronous counter using JK flip flop which can count only odd number with its waveform

- Q5. (2X10=20 Marks) (CO 5)
a. Define RAM and ROM with their types, operation and applications. Implement a PROM for the following Boolean functions:

$$A(x,y,z) = \sum m(5,6,7)$$

$$B(x,y,z) = \sum m(3,5,6,7).$$

- b. Explain the PROM, PAL and PLA programmable logic devices with advantages, limitations and applications.

- c. Realize the following multiple output function using 3 inputs 4 product terms and 2 output PLA:

$$f_1(x,y,z) = \sum m(0,1,3,5)$$

$$f_2(x,y,z) = \sum m(3,5,7)$$