



**End Term (Odd) Semester Examination December 2024**

Roll no. .... 2319126 .....

Name of the Course and semester: B.Tech (III)

Name of the Paper: Logic Design and Computer Organization

Paper Code: TCS 308

Time: 3 hour

Maximum Marks: 100

**Note:**

- (i) All the questions are compulsory.
- (ii) Answer any two sub questions from a, b and c in each main question.
- (iii) Total marks for each question is 20 (twenty). Each sub-question carries 10 marks

Q1.

(2X10=20 Marks) (CO1)

- a. For the given Boolean function:  $f(w,x,y,z) = \sum(0,5,7,8,9,10,14,15)$  find the prime implicants and essential prime implicants using Quine- McClusky method.
- b. Design a combinational circuit that compares two 4-bit numbers, A and B, to check if they are equal. The circuit has one output Y, so that  $Y = 1$  if  $A = B$ , and  $Y = 0$  if  $A \neq B$
- c. Design a 2 bit-magnitude comparator and draw its logic diagram.

Q2.

(2X10=20 Marks) (CO2, CO1)

- a. Perform following flip-flop conversion
  - (i) D to SR
  - (ii) T to JK
- b. Design and explain Universal Shift register.
- c. Design and explain 4 bit Binary Adder- Subtractor.

Q3.

(2X10=20 Marks) (CO3)

- a. A clocked sequential circuit with two D flip flops A and B, an input x and output y. The next State equations for a sequential circuit is given as
$$A(t+1) = Ax + Bx$$
$$B(t+1) = A'x$$
and the present state output are given as,
$$y = (A+B) x'$$
If x is an external input to the sequential circuit
  - (i) Draw the circuit diagram of the sequential circuit.
  - (ii) Obtain state diagram of the sequential circuit.
- b. Design mod-10 synchronous counter using JK-flip flop.
- c. Draw and explain 4 bit Binary ripple Up- Down Counter

Q4.

(2X10=20 Marks) (CO4, CO5)

- a. Differentiate between
  - i) RISC and CISC processors
  - ii) Von Neuman and Harvard Architecture
- b. Discuss Booth algorithm for multiplication with flowchart.
- c. Explain floating point arithmetic operations addition and subtraction with a flowcharts also discuss its hardware implementation.

Q5.

(2X10=20 Marks) (CO6)

- a. Explain the following with flow chart approach
  - i) Interrupt driven I/O
  - ii) Programmed I/O
- b. Discuss memory hierarchy design and its characteristics.
- c. What is DMA? How it works? Explain.