



**Mid Term (Odd) Semester Examination October 2024**

Roll no.....

Name of the Course and semester: B.Tech (CSE) and 3<sup>rd</sup> Semester

Name of the Paper: *Logic Design & Computer Organization*

Paper Code: TCS308

Time: 1.5 hour

Maximum Marks: 50

**Note:**

- (i) Answer all the questions by choosing any one of the sub questions
- (ii) Each question carries 10 marks.

Q1. (10 Marks)  
a. Find the Prime implicants and essential prime implicants of function  $F(A,B,C,D) = \sum m(0, 3, 5, 8, 10, 13)$  using Quine-Mc-Cluskey method. CO1

OR

b. Implement the following Boolean functions using NAND-NAND logic gates? CO1  
(i)  $F = A B + B C + C' D$   
(ii)  $Z = A' B' + A C + B' C'$

Q2. (10 Marks)  
a. Simplify the function  $F(A,B,C,D) = \pi M(4,5,6,7,8,12) + d(0,1,2,3,9,11,14)$  CO2

OR

b. Simplify the function  $F(W,X,Y,Z) = \sum m(0,1,3,5,7,9,11,13,15) + d(8,10,12,14)$  using K-map. CO2

Q3. (10 Marks)  
a. Implement the following function with single 8 x 1 multiplexer where 'D' is a control input

$$F(A,B,C,D) = \sum (0,1,3,4,8,9,15) \quad \text{CO2}$$

OR

b. Implement full adder **SUM** expression using single 4x 1 multiplexer. CO2

Q4. (10 Marks)  
a. Realize the following flip-flops: CO3

- (i) D flip-flop to JK Flip-flop.
- (ii) T flip-flop to D flip-flop.

OR

b. Draw the logic diagram of J K flip-flop and also discuss the functioning of it using characteristic table. CO3

Q5. (10 Marks)  
a. Draw the logic diagram of 4 bit universal shift register and explain its working. CO3

OR

b. Design a 3 bit binary to gray code converter also draw its logic diagram. CO3